

In the given circuit diagram, it is shown that the DC motor, Motor Driver, Keypad, LED LCD, and the buzzer is connected to the LPC2148, where the buzzer buzzes with respect to specified wrong passwords through the keypad to the circuit and the LEDs glow when the correct password is entered and the system opens.

